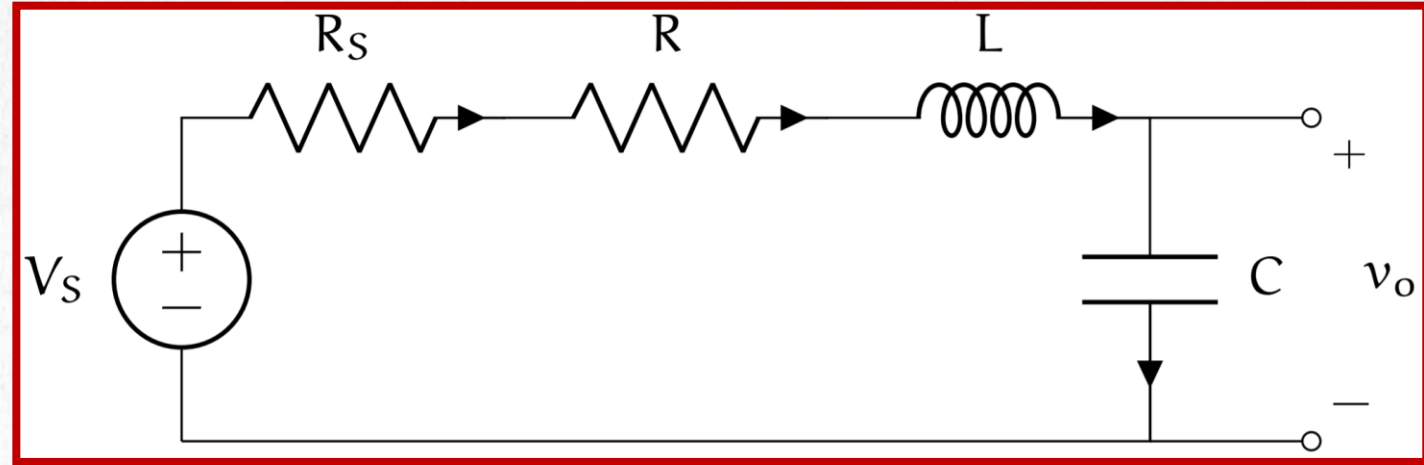


ME316

**Lab 04 – RLC Frequency Response
Prelab**

OVERVIEW


- No LabVIEW this time!
- Use function generators instead
 - Source voltage $V_s - v_{R_s}$
 - Output voltage v_c
 - Phase shift ϕ
- Compare data to frequency response $M(\omega)$ and $\phi(\omega)$ with impedance analysis



RLC circuit diagram

OVERVIEW

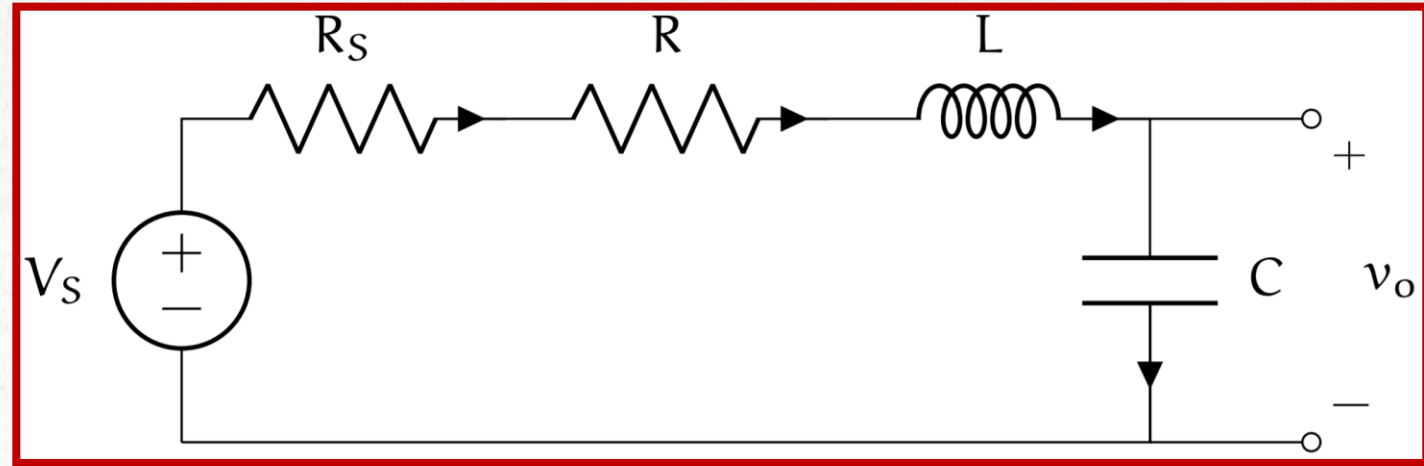- No LabVIEW this time!
- Use function generators instead
 - Source voltage $V_S - v_{R_S}$
 - Output voltage $v_c(\omega)$
 - Phase shift $\phi(\omega)$
- Compare data to frequency response $M(\omega)$ and $\phi(\omega)$ with impedance analysis




RLC circuit diagram

$$\text{Magnitude ratio: } M(\omega) = \frac{v_c}{V_S - v_{R_S}}$$

USING FUNCTION GENERATORS/OSCILLOSCOPES

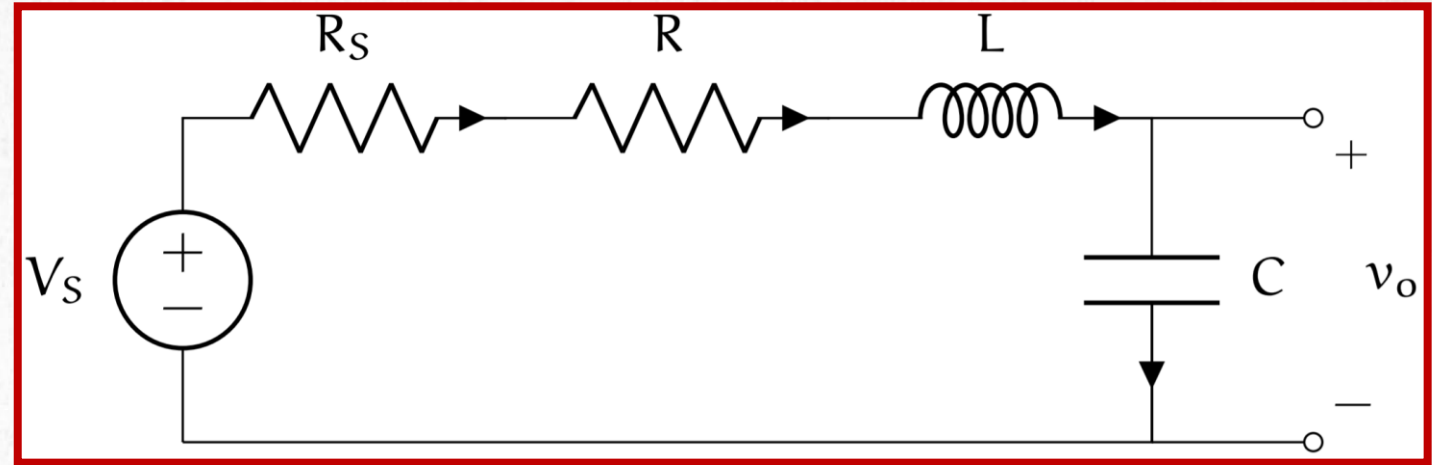- Function generators will **attenuate voltage inputs** without telling you
- In our case, the voltage data is normalized in $M(\omega)$, so our data should be fine



BODE PLOTS

- A way of plotting frequency response for large ranges of ω
- Captures both $M(\omega)$ and $\phi(\omega)$
- You will use this again in **system dynamics** and **control systems**, but in more detail

